

# CompArch Lab 1

William Lu, Kathryn Hite, & Ian Hill

October 6, 2016

## 1 Introduction

We've implemented and tested the arithmetic logic unit subsystem for our new OCA (Olin Computer Architecture) processor.

### 1.1 Circuit Diagram

The final circuit in figure 1 shows each of our final logic modules along with the look up table feeding into the six input multiplexer, giving us the final result of each chosen operation.

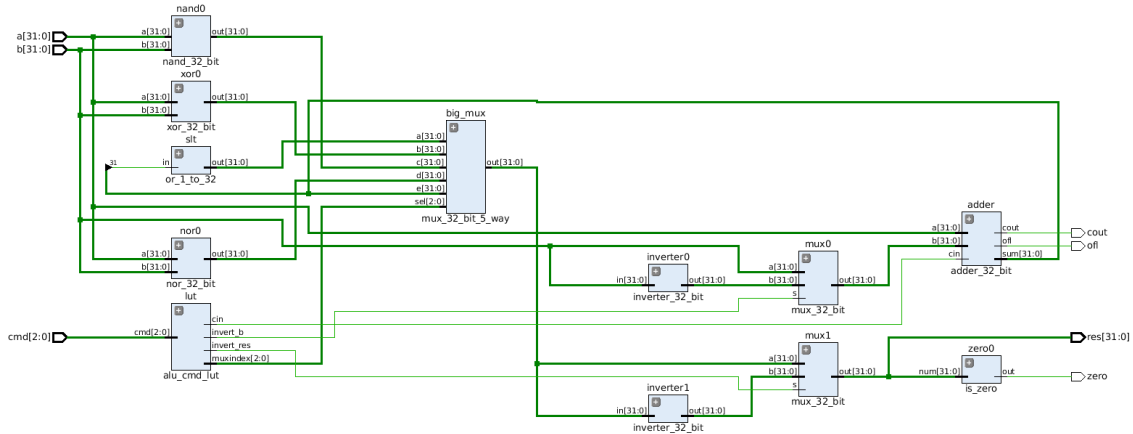


Figure 1: The above schematic is version of our full circuit diagram collapsed for readability.

The full, expanded diagram in figure 2 on the next page, while unreadable, is an interesting illustration of the large number of gates constructing the full modules for each logic and arithmetic operation.

 


Figure 2: The above schematic shows the full, expanded circuit diagram for our ALU.

## 2 Implementation

The implementation of the ALU operation modules structurally followed a bit-slice pattern, but for the sake of code readability and organization, we organized some of the modules into a 1-bit, 8-bit, and 32-bit version.

### 2.1 Command Look Up Table

Per Professor Hill's recommendation, we constructed a LUT in behavior Verilog using a simple switch statement. The LUT set our control signals *muxindex*, *invert\_b*, *invert\_res*, and *cin*. *muxindex* is a 3 bit unsigned integer which controls the primary mux which selects the result of the ALU based on the requested operation. *invert\_b* is a 1 bit flag which changes whether the ALU inverts input *b* before passing it to the adder. *invert\_res* is a 1 bit flag which changes whether the ALU inverts the result of the ALU after it's been selected by the primary mux in order to enable the AND and OR operation which are inversions of NAND and NOR respectively. *cin* is the carry in of the adder which is cleverly set to 1 to enable subtraction after input *b* has been inverted.

## 2.2 Inverter

Our 32 bit inverter (much like our other bitwise operators) was implemented as 32 figure 3 NOT gates in parallel.

 


Figure 3: The 32-bit inverter is comprised of 32 parallel NOT gates.

## 2.3 Adder

The adder was implemented in a bit-slice fashion based on the full adder from our previous lab. These were strung together to form the byte adder shown in figure 4, and four byte adders as seen in figure 5 on the following page were connected to form the 32 bit adder. The full 32 bit adder holds the overflow logic for the adder array.

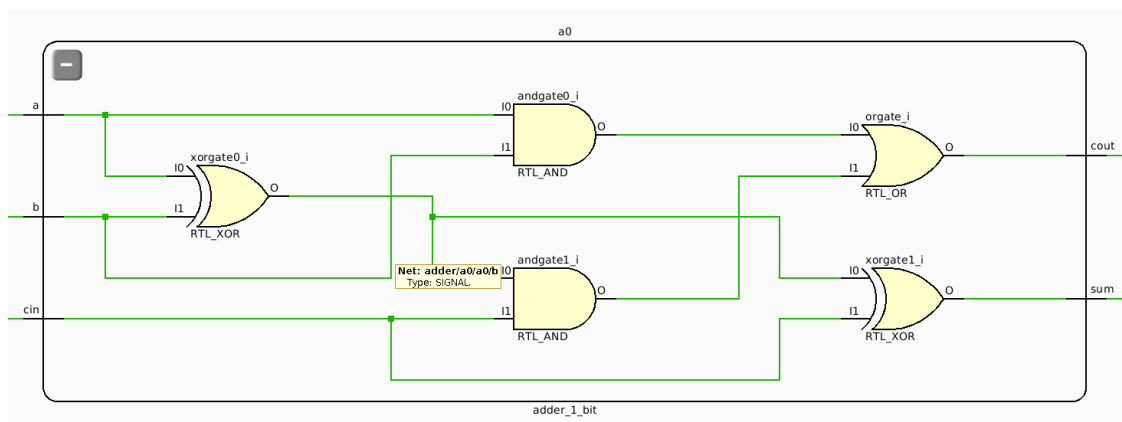


Figure 4: The building block of the full adder implementation is the 1-bit adder module, comprised of five individual gates to compute the sum and carryout.

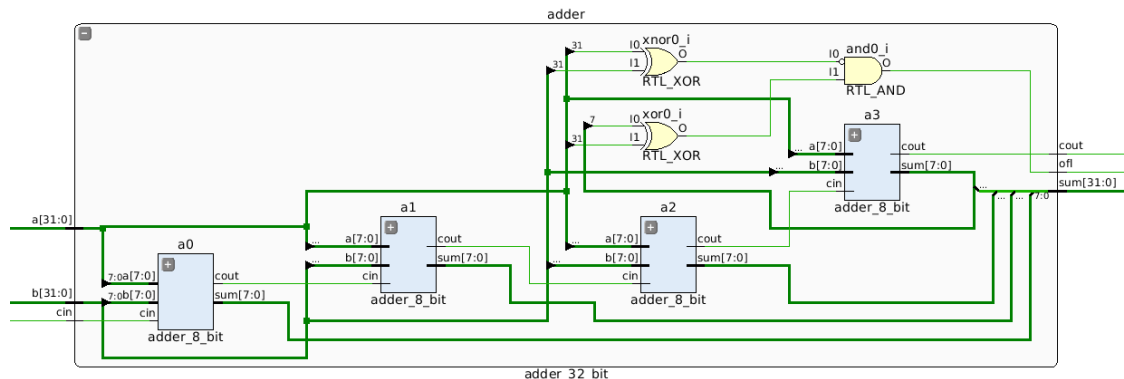


Figure 5: Four of the 1-bit adders are joined to create 4-bit adders. These in turn are strung together to form the final 32-bit adder module.

## 2.4 Subtractor

Subtraction is performed by converting input  $b$  to its opposite and performing normal addition with the adder. To convert input  $b$  to its opposite in 2's complement, the control LUT sets the *invert\_b* flag to invert input  $b$  and sets the *cin* flag to feed the adder a carry in of 1.

## 2.5 Set Less Than

The set less than module takes in two 32-bit strings,  $A$  and  $B$ , and returns a 32-bit string containing all zeros other than the least significant bit. This final bit toggles to 1 if  $A$  is less than  $B$  and is zero otherwise.

The state of the final bit is computed by first inverting  $B$ . Once  $B$  is inverted, we add  $A$  and  $B$  together. If  $A$  is less than  $B$ , the resulting number will be negative as  $B$  was inverted. We can thus take the most significant bit of the adder result as the least significant bit of the slt result. In this case, the less value stored in the least significant bit of the result will be 1 to denote that  $A < B$ .

## 2.6 Bitwise AND, NAND, NOR, and OR

The bitwise AND, NAND, NOR, and OR modules were all built up starting with a single bit version using the defined structural verilog gates given custom delays. Single bit versions were utilized to build up an 8-bit version of each gate bitwise. Four of each of the 8-bit AND, NAND, NOR, and OR modules built up the 32-bit modules using the same method.

 


Figure 6: The 32-bit NOR gate is implemented using four 8-bit NOR modules.

### 3 Tests and Test Results

#### TESTS FOR AND

AND		A: 00000000 00000000 00000000 00000000	B: 00000000 00000000 00000000 00000000
ACT		R: 00000000 00000000 00000000 00000000	
EXP		R: 00000000 00000000 00000000 00000000	
AND		A: 00000000 00000000 00000000 00000000	B: 01111111 11111111 11111111 11111111
ACT		R: 00000000 00000000 00000000 00000000	
EXP		R: 00000000 00000000 00000000 00000000	
AND		A: 01111111 11111111 11111111 11111111	B: 00000000 00000000 00000000 00000000
ACT		R: 00000000 00000000 00000000 00000000	
EXP		R: 00000000 00000000 00000000 00000000	
AND		A: 01111111 11111111 11111111 11111111	B: 01111111 11111111 11111111 11111111
ACT		R: 01111111 11111111 11111111 11111111	
EXP		R: 01111111 11111111 11111111 11111111	
AND		A: 01111111 11111111 11111111 11111111	B: 00000000 10000010 10110110 00110101
ACT		R: 00000000 10000010 10110110 00110101	
EXP		R: 00000000 10000010 10110110 00110101	
AND		A: 00000000 00000000 00000000 00000000	B: 00000000 10000010 10110110 00110101
ACT		R: 00000000 00000000 00000000 00000000	
EXP		R: 00000000 00000000 00000000 00000000	
AND		A: 00000000 10000010 10110110 00110101	B: 00000000 00000000 00000000 00000000

ACT		R:	00000000	00000000	00000000	00000000	
EXP		R:	00000000	00000000	00000000	00000000	
AND		A:	00000000	10000010	10110110	00110101	B: 00000000 10000010 10110110 00110101
ACT		R:	00000000	10000010	10110110	00110101	
EXP		R:	00000000	10000010	10110110	00110101	

#### TESTS FOR NAND

NAND		A:	00000000	00000000	00000000	00000000	B: 00000000 00000000 00000000 00000000
ACT		R:	11111111	11111111	11111111	11111111	
EXP		R:	11111111	11111111	11111111	11111111	
NAND		A:	00000000	00000000	00000000	00000000	B: 01111111 11111111 11111111 11111111
ACT		R:	11111111	11111111	11111111	11111111	
EXP		R:	11111111	11111111	11111111	11111111	
NAND		A:	01111111	11111111	11111111	11111111	B: 00000000 00000000 00000000 00000000
ACT		R:	11111111	11111111	11111111	11111111	
EXP		R:	11111111	11111111	11111111	11111111	
NAND		A:	01111111	11111111	11111111	11111111	B: 01111111 11111111 11111111 11111111
ACT		R:	10000000	00000000	00000000	00000000	
EXP		R:	10000000	00000000	00000000	00000000	
NAND		A:	01111111	11111111	11111111	11111111	B: 00000000 10000010 10110110 00110101
ACT		R:	11111111	01111101	01001001	11001010	
EXP		R:	11111111	01111101	01001001	11001010	
NAND		A:	00000000	00000000	00000000	00000000	B: 00000000 10000010 10110110 00110101
ACT		R:	11111111	11111111	11111111	11111111	
EXP		R:	11111111	11111111	11111111	11111111	
NAND		A:	00000000	10000010	10110110	00110101	B: 00000000 00000000 00000000 00000000
ACT		R:	11111111	11111111	11111111	11111111	
EXP		R:	11111111	11111111	11111111	11111111	
NAND		A:	00000000	10000010	10110110	00110101	B: 00000000 10000010 10110110 00110101
ACT		R:	11111111	01111101	01001001	11001010	
EXP		R:	11111111	01111101	01001001	11001010	

#### TESTS FOR OR

OR		A:	00000000	00000000	00000000	00000000	B: 00000000 00000000 00000000 00000000
ACT		R:	00000000	00000000	00000000	00000000	
EXP		R:	00000000	00000000	00000000	00000000	
OR		A:	00000000	00000000	00000000	00000000	B: 01111111 11111111 11111111 11111111
ACT		R:	01111111	11111111	11111111	11111111	
EXP		R:	01111111	11111111	11111111	11111111	
OR		A:	01111111	11111111	11111111	11111111	B: 00000000 00000000 00000000 00000000
ACT		R:	01111111	11111111	11111111	11111111	
EXP		R:	01111111	11111111	11111111	11111111	
OR		A:	01111111	11111111	11111111	11111111	B: 01111111 11111111 11111111 11111111

ACT		R:	01111111	11111111	11111111	11111111				
EXP		R:	01111111	11111111	11111111	11111111				
OR		A:	01111111	11111111	11111111	11111111	B:	00000000	10000010	10110110 00110101
ACT		R:	01111111	11111111	11111111	11111111				
EXP		R:	01111111	11111111	11111111	11111111				
OR		A:	00000000	00000000	00000000	00000000	B:	00000000	10000010	10110110 00110101
ACT		R:	00000000	10000010	10110110	00110101				
EXP		R:	00000000	10000010	10110110	00110101				
OR		A:	00000000	10000010	10110110	00110101	B:	00000000	00000000	00000000 00000000
ACT		R:	00000000	10000010	10110110	00110101				
EXP		R:	00000000	10000010	10110110	00110101				
OR		A:	00000000	10000010	10110110	00110101	B:	00000000	10000010	10110110 00110101
ACT		R:	00000000	10000010	10110110	00110101				
EXP		R:	00000000	10000010	10110110	00110101				

---

#### TESTS FOR NOR

---

NOR		A:	00000000	00000000	00000000	00000000	B:	00000000	00000000	00000000 00000000
ACT		R:	11111111	11111111	11111111	11111111				
EXP		R:	11111111	11111111	11111111	11111111				
NOR		A:	00000000	00000000	00000000	00000000	B:	01111111	11111111	11111111 11111111
ACT		R:	10000000	00000000	00000000	00000000				
EXP		R:	10000000	00000000	00000000	00000000				
NOR		A:	01111111	11111111	11111111	11111111	B:	00000000	00000000	00000000 00000000
ACT		R:	10000000	00000000	00000000	00000000				
EXP		R:	10000000	00000000	00000000	00000000				
NOR		A:	01111111	11111111	11111111	11111111	B:	01111111	11111111	11111111 11111111
ACT		R:	10000000	00000000	00000000	00000000				
EXP		R:	10000000	00000000	00000000	00000000				
NOR		A:	01111111	11111111	11111111	11111111	B:	00000000	10000010	10110110 00110101
ACT		R:	10000000	00000000	00000000	00000000				
EXP		R:	10000000	00000000	00000000	00000000				
NOR		A:	00000000	00000000	00000000	00000000	B:	00000000	10000010	10110110 00110101
ACT		R:	11111111	01111101	01001001	11001010				
EXP		R:	11111111	01111101	01001001	11001010				
NOR		A:	00000000	10000010	10110110	00110101	B:	00000000	00000000	00000000 00000000
ACT		R:	11111111	01111101	01001001	11001010				
EXP		R:	11111111	01111101	01001001	11001010				
NOR		A:	00000000	10000010	10110110	00110101	B:	00000000	10000010	10110110 00110101
ACT		R:	11111111	01111101	01001001	11001010				
EXP		R:	11111111	01111101	01001001	11001010				

---

#### TESTS FOR XOR

---

XOR		A:	00000000	00000000	00000000	00000000	B:	00000000	00000000	00000000 00000000
-----	--	----	----------	----------	----------	----------	----	----------	----------	-------------------

ACT		R:	00000000	00000000	00000000	00000000	
EXP		R:	00000000	00000000	00000000	00000000	
XOR		A:	00000000	00000000	00000000	00000000	B: 01111111 11111111 11111111 11111111
ACT		R:	01111111	11111111	11111111	11111111	
EXP		R:	01111111	11111111	11111111	11111111	
XOR		A:	01111111	11111111	11111111	11111111	B: 00000000 00000000 00000000 00000000
ACT		R:	01111111	11111111	11111111	11111111	
EXP		R:	01111111	11111111	11111111	11111111	
XOR		A:	01111111	11111111	11111111	11111111	B: 01111111 11111111 11111111 11111111
ACT		R:	00000000	00000000	00000000	00000000	
EXP		R:	00000000	00000000	00000000	00000000	
XOR		A:	01111111	11111111	11111111	11111111	B: 00000000 10000010 10110110 00110101
ACT		R:	01111111	01111101	01001001	11001010	
EXP		R:	01111111	01111101	01001001	11001010	
XOR		A:	00000000	00000000	00000000	00000000	B: 00000000 10000010 10110110 00110101
ACT		R:	00000000	10000010	10110110	00110101	
EXP		R:	00000000	10000010	10110110	00110101	
XOR		A:	00000000	10000010	10110110	00110101	B: 00000000 00000000 00000000 00000000
ACT		R:	00000000	10000010	10110110	00110101	
EXP		R:	00000000	10000010	10110110	00110101	
XOR		A:	00000000	10000010	10110110	00110101	B: 00000000 10000010 10110110 00110101
ACT		R:	00000000	00000000	00000000	00000000	
EXP		R:	00000000	00000000	00000000	00000000	

# TESTS FOR ADDER

ADD		A:	00000000	00000000	00000000	00000000	B: 00000000 00000000 00000000 00000000
ACT		R:	00000000	00000000	00000000	00000000	C: 0 O: 0 Z: 1
EXP		R:	00000000	00000000	00000000	00000000	C: 0 O: 0 Z: 1
ADD		A:	00000000	00000000	00000000	00000001	B: 00000000 00000000 00000000 00000001
ACT		R:	00000000	00000000	00000000	00000010	C: 0 O: 0 Z: 0
EXP		R:	00000000	00000000	00000000	00000010	C: 0 O: 0 Z: 0
ADD		A:	00111111	11111111	11111111	11111111	B: 01000000 00000000 00000000 00000000
ACT		R:	01111111	11111111	11111111	11111111	C: 0 O: 0 Z: 0
EXP		R:	01111111	11111111	11111111	11111111	C: 0 O: 0 Z: 0
ADD		A:	10011001	10011001	10011001	10011001	B: 00010001 00010001 00010001 00010001
ACT		R:	10101010	10101010	10101010	10101010	C: 0 O: 0 Z: 0
EXP		R:	10101010	10101010	10101010	10101010	C: 0 O: 0 Z: 0
ADD		A:	11000000	00000000	00000000	00000000	B: 11000000 00000000 00000000 00000000
ACT		R:	10000000	00000000	00000000	00000000	C: 1 O: 0 Z: 0
EXP		R:	10000000	00000000	00000000	00000000	C: 1 O: 0 Z: 0
ADD		A:	11111111	11111111	11111111	11111111	B: 11111111 11111111 11111111 11111111
ACT		R:	11111111	11111111	11111111	11111110	C: 1 O: 0 Z: 0
EXP		R:	11111111	11111111	11111111	11111110	C: 1 O: 0 Z: 0
ADD		A:	01100110	01100110	01100110	01100110	B: 11111111 11111111 11111111 11111111



ACT		R:	01100110	01100110	01100110	01100101	C:	1	O:	0	Z:	0
EXP		R:	01100110	01100110	01100110	01100101	C:	1	O:	0	Z:	0
ADD		A:	01000000	00000000	00000000	00000000	B:	11000000	00000000	00000000	00000000	
ACT		R:	00000000	00000000	00000000	00000000	C:	1	O:	0	Z:	1
EXP		R:	00000000	00000000	00000000	00000000	C:	1	O:	0	Z:	1
ADD		A:	01000000	00000000	00000000	00000000	B:	01000000	00000000	00000000	00000000	
ACT		R:	10000000	00000000	00000000	00000000	C:	0	O:	1	Z:	0
EXP		R:	10000000	00000000	00000000	00000000	C:	0	O:	1	Z:	0
ADD		A:	01111111	11111111	11111111	11111111	B:	01111111	11111111	11111111	11111111	
ACT		R:	11111111	11111111	11111111	11111110	C:	0	O:	1	Z:	0
EXP		R:	11111111	11111111	11111111	11111110	C:	0	O:	1	Z:	0
ADD		A:	01100110	01100110	01100110	01100110	B:	01111111	11111111	11111111	11111111	
ACT		R:	11100110	01100110	01100110	01100101	C:	0	O:	1	Z:	0
EXP		R:	11100110	01100110	01100110	01100101	C:	0	O:	1	Z:	0
ADD		A:	01010101	01010101	01010101	01010101	B:	01100110	01100110	01100110	01100110	
ACT		R:	10111011	10111011	10111011	10111011	C:	0	O:	1	Z:	0
EXP		R:	10111011	10111011	10111011	10111011	C:	0	O:	1	Z:	0
ADD		A:	10000000	00000000	00000000	00000000	B:	10000000	00000000	00000000	00000000	
ACT		R:	00000000	00000000	00000000	00000000	C:	1	O:	1	Z:	1
EXP		R:	00000000	00000000	00000000	00000000	C:	1	O:	1	Z:	1
ADD		A:	10000000	00000000	00000000	00000000	B:	11111111	11111111	11111111	11111111	
ACT		R:	01111111	11111111	11111111	11111111	C:	1	O:	1	Z:	0
EXP		R:	01111111	11111111	11111111	11111111	C:	1	O:	1	Z:	0
ADD		A:	10101010	10101010	10101010	10101010	B:	10011001	10011001	10011001	10011001	
ACT		R:	01000100	01000100	01000100	01000011	C:	1	O:	1	Z:	0
EXP		R:	01000100	01000100	01000100	01000011	C:	1	O:	1	Z:	0
ADD		A:	10111011	10111011	10111011	10111011	B:	10101010	10101010	10101010	10101010	
ACT		R:	01100110	01100110	01100110	01100101	C:	1	O:	1	Z:	0
EXP		R:	01100110	01100110	01100110	01100101	C:	1	O:	1	Z:	0

---

#### TESTS FOR SUBTRACTOR

---

SUB		A:	00000000	00000000	00000000	00000000	B:	00000000	00000000	00000000	00000000	
ACT		R:	00000000	00000000	00000000	00000000	C:	1	O:	0	Z:	1
EXP		R:	00000000	00000000	00000000	00000000	C:	1	O:	0	Z:	1
SUB		A:	00000000	00000000	00000000	00000001	B:	00000000	00000000	00000000	00000001	
ACT		R:	00000000	00000000	00000000	00000000	C:	1	O:	0	Z:	1
EXP		R:	00000000	00000000	00000000	00000000	C:	1	O:	0	Z:	1
SUB		A:	01111111	11111111	11111111	11111111	B:	00000000	00000000	00000000	00000001	
ACT		R:	01111111	11111111	11111111	11111110	C:	1	O:	0	Z:	0
EXP		R:	01111111	11111111	11111111	11111110	C:	1	O:	0	Z:	0
SUB		A:	00000000	00000000	00000000	00000001	B:	01111111	11111111	11111111	11111111	
ACT		R:	10000000	00000000	00000000	00000010	C:	0	O:	0	Z:	0
EXP		R:	10000000	00000000	00000000	00000010	C:	0	O:	0	Z:	0

---

## TESTS FOR SLT

```

SLT  | A: 00000000 00000000 00000000 00000000 B: 00000000 00000000 00000000 00000000
    ACT | R: 00000000 00000000 00000000 00000000 C: 1 0: 0 Z: 1
    EXP | R: 00000000 00000000 00000000 00000000 C: 1 0: 0 Z: 1
SLT  | A: 01111111 11111111 11111111 11111111 B: 00000000 00000000 00000000 00000000
    ACT | R: 00000000 00000000 00000000 00000000 C: 1 0: 0 Z: 1
    EXP | R: 00000000 00000000 00000000 00000000 C: 1 0: 0 Z: 1
SLT  | A: 00000000 00000000 00000000 00000000 B: 01111111 11111111 11111111 11111111
    ACT | R: 00000000 00000000 00000000 00000001 C: 0 0: 0 Z: 0
    EXP | R: 00000000 00000000 00000000 00000001 C: 0 0: 0 Z: 0
SLT  | A: 01111111 11111111 11111111 11111111 B: 00000000 10000010 10110110 00110101
    ACT | R: 00000000 00000000 00000000 00000000 C: 1 0: 0 Z: 1
    EXP | R: 00000000 00000000 00000000 00000000 C: 1 0: 0 Z: 1
SLT  | A: 00000000 10000010 10110110 00110101 B: 01111111 11111111 11111111 11111111
    ACT | R: 00000000 00000000 00000000 00000001 C: 0 0: 0 Z: 0
    EXP | R: 00000000 00000000 00000000 00000001 C: 0 0: 0 Z: 0
SLT  | A: 11111111 01111101 01001001 11001011 B: 00000000 10000010 10110110 00110101
    ACT | R: 00000000 00000000 00000000 00000001 C: 1 0: 0 Z: 0
    EXP | R: 00000000 00000000 00000000 00000001 C: 1 0: 0 Z: 0
SLT  | A: 11111111 01111101 01001001 11001011 B: 00000000 00000000 00000000 00000000
    ACT | R: 00000000 00000000 00000000 00000001 C: 1 0: 0 Z: 0
    EXP | R: 00000000 00000000 00000000 00000001 C: 1 0: 0 Z: 0
SLT  | A: 11111111 01111101 01001001 11001011 B: 10000000 00000000 00000000 00000001
    ACT | R: 00000000 00000000 00000000 00000000 C: 1 0: 0 Z: 1
    EXP | R: 00000000 00000000 00000000 00000000 C: 1 0: 0 Z: 1
SLT  | A: 10000000 00000000 00000000 00000001 B: 11111111 01111101 01001001 11001011
    ACT | R: 00000000 00000000 00000000 00000001 C: 0 0: 0 Z: 0
    EXP | R: 00000000 00000000 00000000 00000001 C: 0 0: 0 Z: 0
SLT  | A: 11111111 01111101 01001001 11001011 B: 01111111 11111111 11111111 11111111
    ACT | R: 00000000 00000000 00000000 00000000 C: 1 0: 1 Z: 1
    EXP | R: 00000000 00000000 00000000 00000000 C: 1 0: 1 Z: 1

```

Listing 1: Text results for the ALU.

## 3.1 Results

Our comprehensive but non-exhaustive tests show that our ALU functions as expected. Each of the “basic” gates (AND, NAND, OR, NOR, XOR) function properly, and the adder, subtractor, and SLT behave as expected. Tests were chosen to evaluate edge cases (e.g. 0, large numbers, negative computations) as well as more “normal” scenarios (e.g. numbers that are not 0 and  $2147483647_{10}$ ).

Because the SLT is based off of the 32 bit adder in our ALU, comparing two numbers that are large in magnitude cause overflow, resulting in an invalid comparison.

## 4 Timing Analysis

The results of the timing analysis are shown in table 1. The worst case propagation delay is 4060 time units and occurs in the SLT path. The main reason for this large delay is the adder module, which is a propagation of 32 modules requiring 120 time units each.

Table 1: ALU Module Timing Analysis

Module	Compenent Timing	Total
SUB	$70 + 3840 + 70 + 70$	4050
SUB	$\text{ADD} + 10$	4060
SLT	$\text{SUB} + 30 + 210$	240
NAND	$20 + 210 + 70$	300
AND	$\text{NAND} + 10$	400
NOR	$20 + 210 + 170$	400
OR	$\text{NOR} + 10$	410
XOR	$60 + 210 + 70$	420

## 5 Work Plan Reflection

### 5.1 Work Plan

-----  
CompArch Lab 1 Work Plan  
-----

- (1.5) Build test bench
  - (1) Finding and choosing appropriate test cases
- (0.5) Implement test cases
- (3) Build modules
  - (1) AND, NAND, NOR, OR
  - (1) Adder, Subtractor
  - (1) SLT
- (2.5) Report

William: Start coming up with test cases

Ian: Start writing the test bench

William: Write AND, NAND, NOR, OR modules

Katie: Write Adder, Subtractor, and SLT modules

Everyone: Write report  
-----

## Notes

---

### Verilog module

- Adder: reuse 4 bit adder from Lab1
- Subtractor: tweak 4 bit adder from Lab1
- XOR: Modified OR gate
- SLT: Build 1 bit, string 32 of them together
- AND: Use structural AND
- NAND: Use structural NAND
- NOR: Use structural NOR
- OR: Use structural OR

### Test bench

- Test cases
- Implementation

### Report

- Implementation
- Test Results
- Timing analysis
- Reflection

## 5.2 Reflection

The total times spent on each portion of the work plan deviated from our initial estimates as follows:

### (1.5) Build test bench

#### (1) Finding and choosing appropriate test cases

It took 2 hours rather than the initial estimate of 1 to select appropriate test cases for each of the modules.

#### (0.5) Implement test cases

Implementing the test case file also took approximately double the estimated time to complete.

### (3) Build modules

The amount of time spent building the individual modules totaled to 5 hours. The initial estimate of 3 hours total for the three subsets of modules did not take into consideration aspects including the main ALU module and updating the timing of the structural verilog gates.

### (2.5) Report

Generating the documentation, figures, and explanations for the report was approximately within the time given in our workplan.